


ECE202 Electrical Networks

Homework #4


Assigned: Thursday, February 8th 2007

Due: Thursday, February 15th 2007

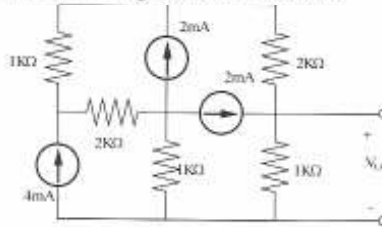
1. Find V_o in the circuit shown using Thevenin's Theorem.



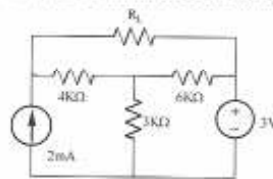
2. In the network shown using Thevenin's theorem find R_L for maximum power transfer and the maximum power that can be transferred to this load.



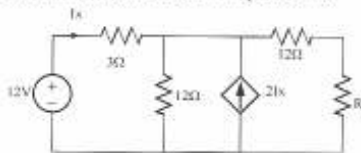
3. Find the value of R_L in the network shown for maximum power transfer to this load. Use Norton's theorem for the solution of this problem.



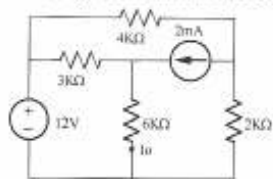
4. Find I_o in the network shown using Thevenin's Theorem.




Solutions to HW #4

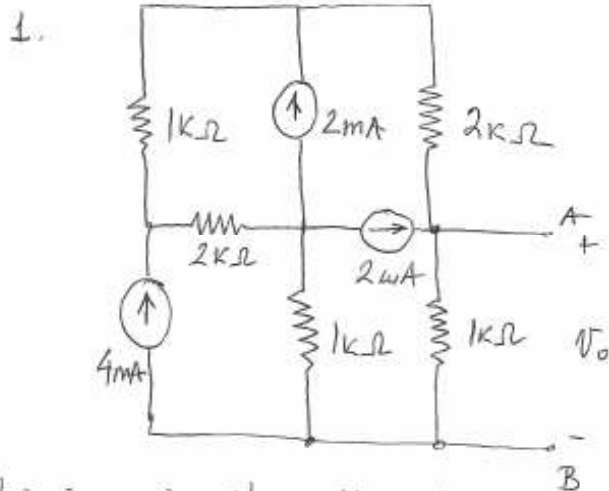

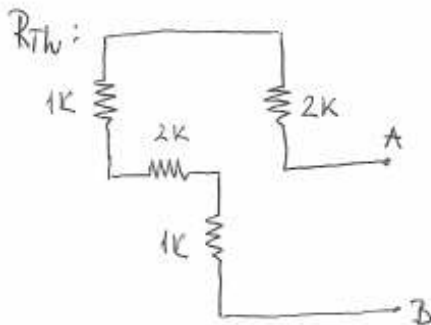This is a circuit with independent sources only and we need only to calculate R_{Th} and V_{oc} . We disconnect the $1k\Omega$ resistor between nodes A and B.



$$R_{Th} = 2k + 2k + 1k + 1k = 6k$$

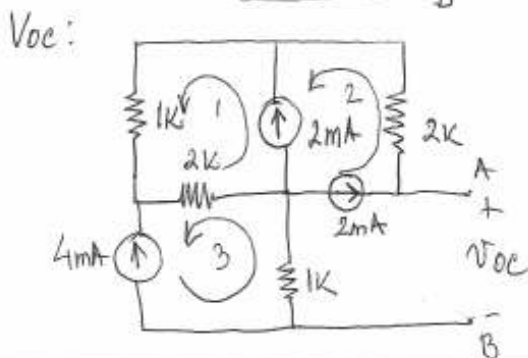


$$I_1 - I_2 = 2mA$$

$$I_2 = 2\mu A \quad I_1 = 4\mu A$$

$$I_3 = -4\mu A$$


$$V_{oc} = 2kI_2 + 1kI_1 + 2k(I_1 - I_3) - 1kI_3$$
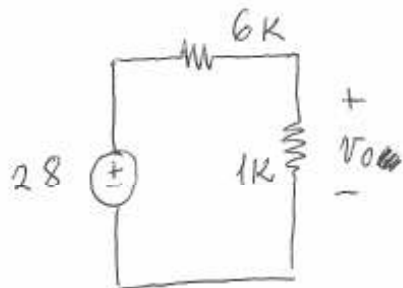
$$V_{oc} = 2k \times 2m + 1k \times 4m + 2k(4m + 4m) + 1k \cdot 4m = 4 + 4 + 16 + 4 = 28V$$




$$V_o = 28 \cdot \frac{1}{6+1} = \frac{28}{7} = 4V$$

2.

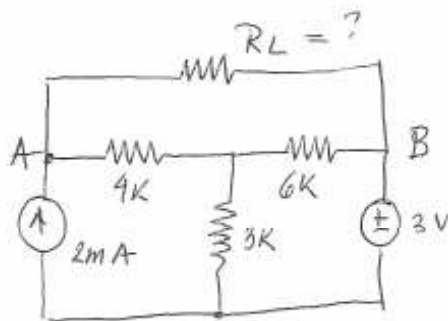


$R_L = ?$ for maximum power transfer + we have to calculate maximum power transferred.

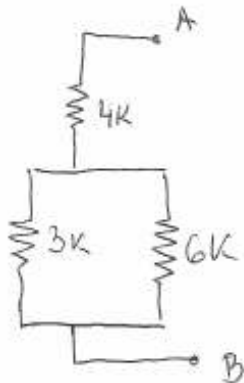This is also a Type 1 circuit since it only has independent voltage sources so we need to calculate the open circuit voltage V_{oc} and thevenin's Resistance


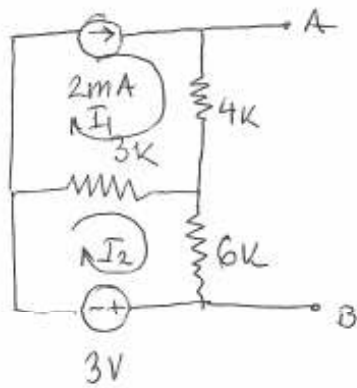
$$R_{Th} = 4k + \frac{6k \cdot 3k}{9k} = 6k$$



$$I_1 = 2 \text{ mA}$$

$$3\text{k}(I_2 - I_1) + 6\text{k}I_2 + 3 = 0$$

$$9\text{k}I_2 + 3 - 6 = 0$$


$$9\text{k}I_2 = 3$$

$$I_2 = \frac{1}{3} \text{ mA}$$

$$V_{oc} = 4\text{k}I_1 + 6\text{k}I_2 = 4\text{k} \times 2\text{m} + 6\text{k} \times \frac{1}{3}\text{m} = 10 \text{ V}$$

The condition for maximum power transfer is


$$R_L = R_{TH} = 6\text{k}$$

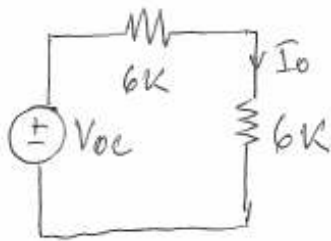

$$I_0 = \frac{10}{12\text{k}} = \frac{5}{6} \text{ mA}$$

$$P_{max} = V_0 I_0 = R_L I_0^2 = 6\text{k} \left(\frac{5}{6}\text{m}\right)^2 = \frac{25}{6} \text{ mW}$$

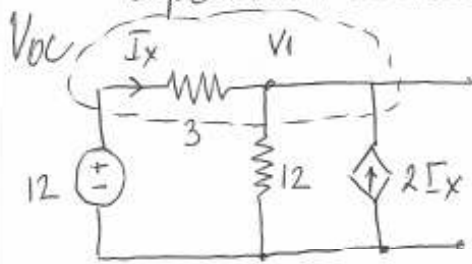3. We have a circuit with both independent and dependent sources so $R_{Th} = V_{oc} / I_{sc}$




$$\frac{V_1}{12} - 2I_x - I_x = 0$$

$$\frac{V_1}{12} - 3I_x = 0$$

$$I_x = \frac{12 - V_1}{3} \Rightarrow \frac{V_1}{12} - 3 \cdot \frac{12 - V_1}{3} = 0$$

$$\frac{V_1}{12} - 12 + V_1 = 0$$
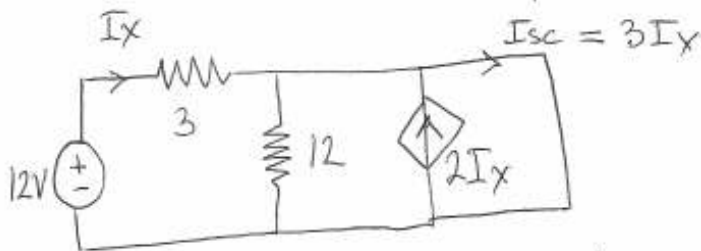
$$\frac{13}{12} V_1 = 12 \quad V_1 = \frac{144}{13} = V_{oc}$$




$$12V = 3I_x \quad I_x = 12/3 = 4A \quad I_{sc} = 12A$$

$$R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{144}{13 \times 12} = \frac{12}{13}$$

$$R_L = R_{Th} + 12 \Omega = \frac{12}{13} + 12 = \frac{168}{13} = 12.923 \Omega$$

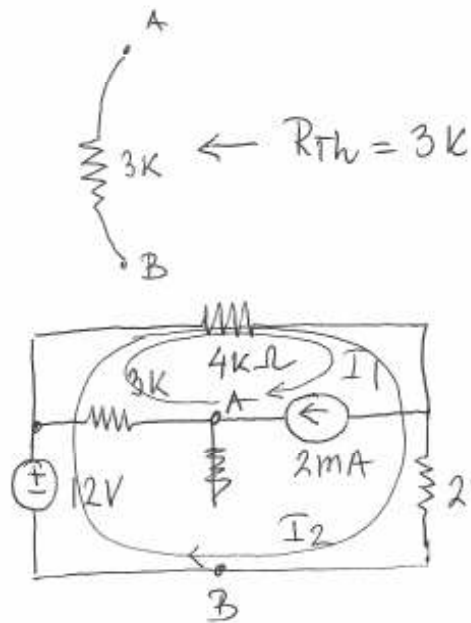4. This is Type I circuit for independent voltage sources so we need to calculate V_{oc} and R_{Th} . Disconnect the $6k$ resistor.




$$I_1 = 2 \text{ mA}$$

$$-12 + 4k(I_1 + I_2) + 2kI_2 = 0$$

$$-12 + 6kI_2 + 8 = 0$$

$$6kI_2 = 4 \Rightarrow I_2 = \frac{2}{3} \text{ mA}$$
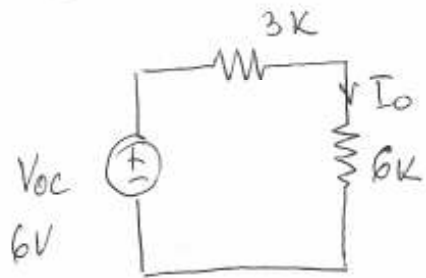
$$V_{oc} = V_{AB} = -3k(I_1 + I_2) + 12V = 12 - 3k \times 2m = 6V$$



$$I_0 = \frac{6}{9k} = \frac{2}{3} \text{ mA}$$