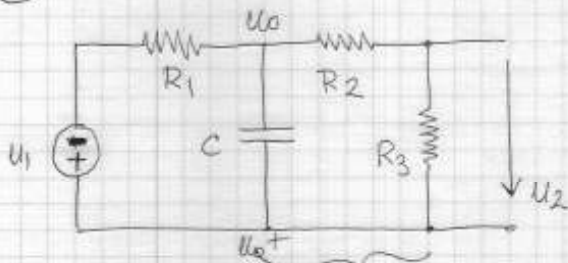


$$R_1 = 1k, R_2 = 2k, L_1 = 0.1H \\ C = 10^{-6}$$

$$\begin{aligned} \frac{U_2(s)}{U_1(s)} &= \frac{R_2 + sL_1}{R_2 + sL_1 + \frac{R_1 \cdot 1/sC}{R_1 + \frac{1}{sC}}} \\ &= \frac{R_2 + sL_1}{R_2 + sL_1 + \frac{R_1}{1 + sCR_1}} \\ &= \frac{(R_2 + sL_1)(1 + sCR_1)}{R_1 + (R_2 + sL_1)(1 + sCR_1)} \end{aligned}$$

② $U_1(t) = U_0 + U_{m1} \sin(\omega_0 t + \varphi_1) + U_{m3} \sin(3\omega_0 t + \varphi_3)$



$$R_1 = 1k\Omega, R_2 = 2k\Omega \\ R_3 = 4k\Omega, C = 1\mu F \\ U_0 = 5V, U_{m1} = 10V, U_{m3} = 2V \\ \omega_0 = 1000 \text{ rad/s}, \varphi_1 = -\pi/4, \varphi_3 = -\pi/3$$

$$Z_2 = \frac{1}{j\omega C} (R_2 + R_3) = \frac{R_2 + R_3}{1 + j\omega C (R_2 + R_3)}$$

$$U_0 = \frac{Z_2 U_1}{R_1 + Z_2} = \frac{R_2 + R_3}{R_1 + \frac{R_2 + R_3}{1 + j\omega C (R_2 + R_3)}} U_1 = \frac{(R_2 + R_3) U_1}{R_1 (1 + j\omega C (R_2 + R_3)) + R_2 + R_3}$$

$$= \frac{R_2 + R_3}{R_1 + R_2 + R_3 + j\omega C (R_2 + R_3) R_1} U_1$$

$$U_2 = \frac{R_3}{R_2 + R_3} U_0 = \frac{R_3 U_1}{R_1 + R_2 + R_3 + j\omega C (R_2 + R_3) R_1}$$

$$U_2 = \frac{R_3 U_1}{R_1 + R_2 + R_3 + j\omega C R_1 (R_2 + R_3)}$$

$$U_2 = \frac{4K U_1}{1K + 2K + 4K + j\omega 1K \cdot 1K \cdot 1\mu (2K + 4K)} =$$

$$= \frac{4K U_1}{7K + j\omega 6K} = \frac{4}{7 + j6\omega} U_1$$

$$1) U_1 = U_0, \omega = 0, n = 0 \quad U_2 = \frac{4}{7} \cdot 5 = \frac{20}{7}$$

$$2) U_1 = U_{m1}, \omega = \omega_0, n = 1 \quad U_2 = \frac{4}{7 + j6} 10 \angle \bar{u}/4 =$$

$$= \frac{40}{\sqrt{49 + 36}} \angle \bar{u}/4 - \tan^{-1}\left(\frac{6}{7}\right)$$

$$= \frac{40}{\sqrt{85}} \angle \bar{u}/4 - \tan^{-1}\left(\frac{6}{7}\right) = U_{02} \angle \theta_2$$

$$3) U_3 = U_{m3}, \omega = 3\omega_0, n = 3 \quad U_3 = \frac{4}{7 + j18} 2 \angle -\bar{u}/3$$


$$U_3 = \frac{8}{\sqrt{49 + 18^2}} \angle -\bar{u}/3 - \tan^{-1}\left(\frac{18}{7}\right) = U_{03} \angle \theta_3$$

$$u_2(t) = \frac{20}{7} + \frac{40}{\sqrt{85}} \sin(\omega_0 t + \bar{u}/4 - \tan^{-1}(6/7))$$

$$+ \frac{8}{\sqrt{49 + 18^2}} \sin(3\omega_0 t - \bar{u}/3 - \tan^{-1}(18/7))$$

$$U_{\text{rms}} = \frac{1}{\sqrt{2}} \sqrt{\left(\frac{20}{7}\right)^2 + \frac{40^2}{85} + \frac{64}{49 + 18^2}}$$
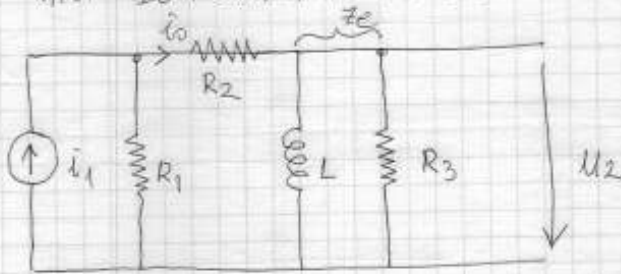
$$③ \quad i_1(t) = I_0 + I_{m1} \sin(\omega_0 t + \varphi_1) + I_{m3} \sin(3\omega_0 t + \varphi_3)$$



$$R_1 = 1k, R_2 = 2k, R_3 = 4k, L = 1H$$

$$I_0 = 5mA, I_{m1} = 10mA, I_{m3} = 2mA$$

$$\omega_0 = 1000 \text{ rad/s}, \varphi_1 = \pi/4, \varphi_3 = -\pi/3$$

$$Z_e = \frac{R_3 \cdot j\omega L}{R_3 + j\omega L} = \frac{j\omega L R_3}{R_3 + j\omega L}$$

$$I_0 = \frac{R_1}{R_1 + R_2 + \frac{j\omega L R_3}{R_3 + j\omega L}} = \frac{R_1(R_3 + j\omega L)}{(R_1 + R_2)(R_3 + j\omega L) + j\omega L R_3} I_1$$

$$u_2 = \frac{j\omega L R_3}{R_3 + j\omega L} \frac{R_1(R_3 + j\omega L)}{(R_1 + R_2)(R_3 + j\omega L) + j\omega L R_3} I_1$$

$$u_2 = \frac{j\omega L R_1 R_3}{(R_1 + R_2)(R_3 + j\omega L) + j\omega L R_3} I_1$$

$$u_2 = \frac{j1k \cdot 1k \cdot 4k \text{ n}}{3k(4k + j1k \text{ n})} I_1 = \frac{j4k \text{ n}}{3(4 + j1 \text{ n})} I_1$$

$$1) \bar{I}_1 = I_0 = 5 \text{ mA}, \omega = 0, n = 0 \quad U_2 = 0$$

$$2) \bar{I}_2 = I_{m1} = 10 \text{ mA} \quad \underline{\bar{v}/4} \quad n = 1$$

$$U_{22} = \frac{j4 \cancel{\text{K}} \cdot 10 \text{ mA} \underline{\bar{v}/4}}{3(4+j)} = \frac{40 \underline{\bar{v}/4 + \bar{v}/2}}{3\sqrt{17} \underline{\tan^{-1}(1/4)}}$$

$$U_{22} = \frac{40}{3\sqrt{17}} \underline{\bar{v}/4 + \bar{v}/2 - \tan^{-1}(1/4)}$$

$$3) \bar{I}_3 = I_{m3} = 2 \text{ mA} \quad \underline{-\bar{v}/3}$$


$$U_{23} = \frac{j4 \times 3 \times 2 \underline{-\bar{v}/3}}{3(4+j3)} = \frac{24 \cdot 8}{3\sqrt{16+9}} \underline{\bar{v}/2 - \bar{v}/3 - \tan^{-1}(3/4)}$$

$$U_{23} = \frac{8}{5} \underline{\bar{v}/2 - \bar{v}/3 - \tan^{-1}(3/4)}$$

$$U_2(t) = \frac{40}{3\sqrt{17}} \sin(\omega_0 t + \bar{v}/4 + \bar{v}/2 - \tan^{-1}(1/4))$$

$$+ \frac{8}{5} \sin(\beta \omega_0 t + \bar{v}/2 - \bar{v}/3 - \tan^{-1}(3/4)) \quad \checkmark$$
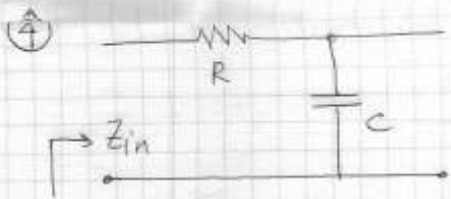
$$U_{2\text{rms}} = \frac{1}{\sqrt{2}} \sqrt{\left(\frac{40}{3\sqrt{17}}\right)^2 + \left(\frac{8}{5}\right)^2}$$



1) Impedance

$$\underline{Z} = R + \frac{1}{j\omega C} = R - j\frac{1}{\omega C}$$


2) $v(t) = v e^{j\omega t}$ $V = v \angle 0$

$$I_c = \frac{V}{\underline{Z}} = \frac{v \angle 0}{\sqrt{R + (\frac{1}{\omega C})^2} \angle -\tan^{-1}(\frac{1}{\omega RC})} = \frac{v}{\sqrt{R + (\frac{1}{\omega C})^2}} \angle \tan^{-1}(\frac{1}{\omega RC})$$

$$i_c = \frac{v}{\sqrt{R + (\frac{1}{\omega C})^2}} \cos(\omega t + \tan^{-1}(\frac{1}{\omega RC}))$$

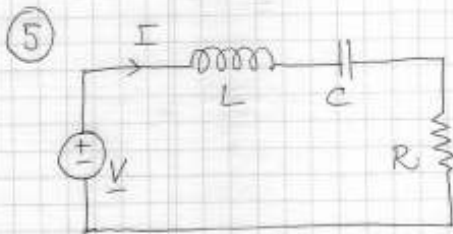3) $V_c = \frac{1}{j\omega C} I_c = \frac{1}{j\omega C} \frac{v}{\sqrt{R + (\frac{1}{\omega C})^2}} \angle \tan^{-1}(\frac{1}{\omega RC})$

$$\theta = \tan^{-1}(\frac{1}{\omega RC}) - \frac{\pi}{2}$$



$\omega = 1 \text{ k rad/s}$ $R = 1 \text{ k}\Omega$, $L = 1 \text{ H}$
 $C = 10 \text{ nF}$

(1) $I = \frac{V}{R + j(\omega L - \frac{1}{\omega C})}$

$$|I| = \frac{V_0}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

(2) $\varphi_I = -\tan^{-1}\left(\frac{\omega L - \frac{1}{\omega C}}{R}\right)$

(3) $U_L = j\omega L I$ $|U_L| = \frac{\omega L V_0}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$

(4) $\theta_L = \pi/2 - \tan^{-1}\left(\frac{\omega L - \frac{1}{\omega C}}{R}\right)$ (5) $\omega = \frac{1}{\sqrt{LC}}$