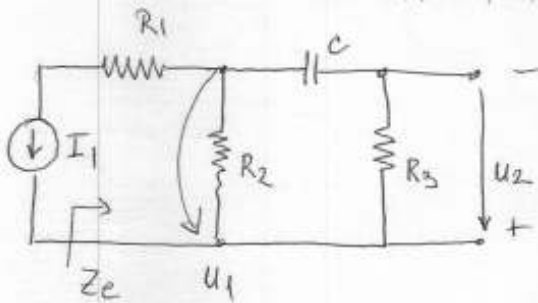


$R_1 = 1 \text{ k}\Omega, R_2 = 2 \text{ k}\Omega, R_3 = 4 \text{ k}\Omega, C = 1 \mu\text{F},$
 $U_0 = 5 \text{ V}, U_{m1} = 10 \text{ V}, U_{m2} = 2 \text{ V},$
 $\omega_0 = 1000 \text{ s}^{-1}, \varphi_1 = 1/4 \pi, \varphi_2 = -1/3 \pi$



$$Z_e = \frac{R_2 (R_3 + \frac{1}{j\omega C})}{R_2 + R_3 + \frac{1}{j\omega C}} = \frac{R_2 (1 + j\omega C R_3)}{1 + j\omega C (R_2 + R_3)}$$

$$U_1 = Z_e I_1 \quad U_2 = \frac{R_3}{R_3 + \frac{1}{j\omega C}} U_1 = \frac{j\omega C R_3}{1 + j\omega C R_3} U_1$$

$$U_2 = \frac{j\omega C R_3}{1 + j\omega C R_3} \cdot \frac{R_2 (1 + j\omega C R_3)}{1 + j\omega C (R_2 + R_3)} I_1$$

Where $\underline{I}_1 = 5 + 10 \sin(\omega_0 t + \bar{u}/4) + 2 \sin(3\omega_0 t - \bar{u}/3)$

DC component $\omega = 0$

$U_{2DC} = 0$ capacitor prevents current flow

1st AC component

$$I_1 = 10 \angle \bar{u}/4 (\omega_0)$$

2nd AC component

$$I_2 = 2 \angle -\bar{u}/3 (3\omega_0)$$

$$\begin{aligned}
 U_2 &= \frac{j\omega 10^{-6} 4k}{1 + j\omega 10^{-6} 4k} \cdot \frac{2k(1 + j\omega 10^{-6} 4k)}{1 + j\omega 10^{-6}(2k + 1k)} I_1 \\
 &= \frac{j4\omega k}{1 + j4\omega m} \cdot \frac{2k(1 + j\omega 4m)}{1 + j\omega \cdot 3m} I_1 \\
 &= \frac{j4\omega}{1 + j4\omega m} \cdot \frac{2(1 + j4\omega m)}{1 + j3\omega m} I_1
 \end{aligned}$$

when $\omega = \omega_0 = 1k$ and $I_1 = 10/\sqrt{4}$

$$U_{2\omega} = \frac{j4}{1 + j4} \cdot \frac{2(1 + j4)}{1 + j3} \cdot 10 \frac{\sqrt{2}}{2} (1 + j)$$

when $\omega = 3\omega_0 = 3k$ and $I_2 = 2 e^{-j\sqrt{3}/3}$

$$U_{2(3\omega)} = \frac{j12}{1 + j12} \cdot \frac{2(1 + j12)}{1 + j9} \cdot 2 e^{-j\sqrt{3}/3}$$

Then


$$U_2 = U_{2\omega} + U_{23\omega}$$

↓ convert each term in real space


$$U_2(t) = U_{21} \cos(\omega_0 t + \theta_1) + U_{22} \cos(3\omega_0 t + \theta_3)$$

$$U_{2rms} = \sqrt{U_{21}^2 + U_{22}^2}$$

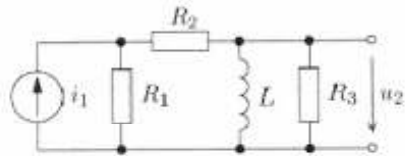Circuits shown in the two figures below are supplied by the periodic non-sinusoidal current $i_1(t) = I_0 + I_{m1} \sin(\omega_0 t + \varphi_1) + I_{m3} \sin(3\omega_0 t + \varphi_3)$ and they are in the steady state. Find the output voltage $u_2(t)$ and its effective (rms) value U_2


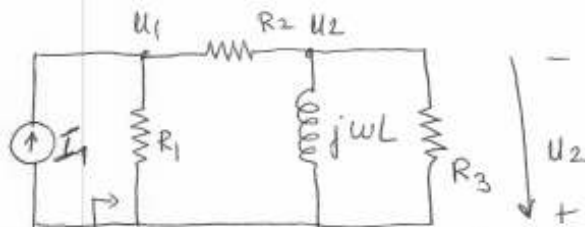
$$R_1 = 1 \text{ k}\Omega, R_2 = 2 \text{ k}\Omega, R_3 = 4 \text{ k}\Omega, L = 1 \text{ H}, \\ I_0 = 5 \text{ mA}, I_{m1} = 10 \text{ mA}, I_{m3} = 2 \text{ mA}, \\ \omega_0 = 1000 \text{ s}^{-1}, \varphi_1 = 1/4 \pi, \varphi_3 = -1/3 \pi$$



$$Z_e = \frac{R_1 \left(R_2 + \frac{R_3 j\omega L}{R_3 + j\omega L} \right)}{R_1 + R_2 + \frac{R_3 j\omega L}{R_3 + j\omega L}} = \frac{R_1 (R_2 (R_3 + j\omega L) + R_3 j\omega L)}{(R_1 + R_2)(R_3 + j\omega L) + R_3 j\omega L}$$

$$Z_e = \frac{R_1 R_2 R_3 + j\omega L (R_3 R_1 + R_2 R_1)}{(R_1 + R_2) R_3 + j\omega L (R_1 + R_2 + R_3)}$$

$$u_1 = Z_e I_1$$

$$u_2 = - \frac{\frac{R_3 j\omega L}{R_3 + j\omega L} u_1}{R_2 + \frac{R_3 j\omega L}{R_3 + j\omega L}} = - \frac{j\omega L R_3 u_1}{R_2 (R_3 + j\omega L) + R_3 j\omega L} = \frac{-j\omega L R_3 u_1}{R_2 R_3 + j\omega L (R_2 + R_3)}$$

$$u_2 = - \frac{j\omega L R_3}{R_2 R_3 + j\omega L (R_2 + R_3)} \cdot \frac{R_1 R_2 R_3 + j\omega L (R_3 + R_2) R_1}{(R_1 + R_2) R_3 + j\omega L (R_1 + R_2 + R_3)} I_1$$

$$u_2 = -\frac{j\omega 4k}{8k + j\omega(4+2)k} \cdot \frac{8k + j\omega(6k) \cdot 1k}{3k \cdot 4k + j\omega(7k)m} I_1$$

$$= \frac{-j4\omega}{8k + j6\omega} \cdot \frac{8k + j6\omega}{12 + j7\omega m} I_1$$

Now:


$$1) \omega = \omega_0 = 1000 \text{ s}^{-1} = 1k \quad I_1 = I_{m1} e^{j\varphi_1}$$

$$u_2 = -\frac{j4k}{8k + j6k} \cdot \frac{8k + j6k}{1 + j7} I_{m1} e^{j\varphi_1}$$

$$2) \omega = 3\omega_0 = 3k \text{ s}^{-1} \quad I_1 = I_{m3} e^{j\varphi_3}$$

$$u_2 = -\frac{j12k}{8k + j18k} \cdot \frac{8k + j18k}{12 + j21} \frac{I_{e3}}{m^0} e^{j\varphi_3} = -\frac{j12k}{12 + j21} I_{m3} e^{j\varphi_3}$$

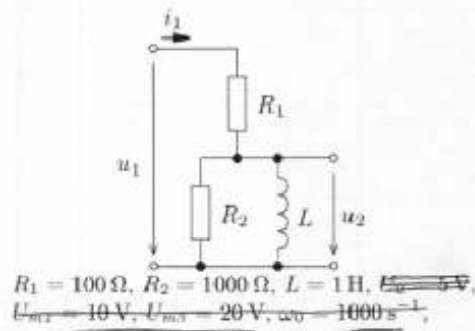convert each into real time and add real time quantities




Transfer function calculation:

$$Z_e = \frac{R_2 j\omega L}{R_2 + j\omega L}$$

$$H(\omega) = \frac{U_2(\omega)}{U_1(\omega)} = \frac{Z_e}{R_1 + Z_e} = \frac{\frac{R_2 j\omega L}{R_2 + j\omega L}}{R_1 + \frac{R_2 j\omega L}{R_2 + j\omega L}} = \frac{j\omega L R_2}{R_1(R_2 + j\omega L) + j\omega L R_2}$$

$$H(\omega) = \frac{j\omega 1\text{K}}{0.1\text{K}(1\text{K} + j\omega) + j\omega \cdot 1\text{K}} = \frac{j\omega}{0.1\text{K} + j\omega(1 + 0.1)}$$
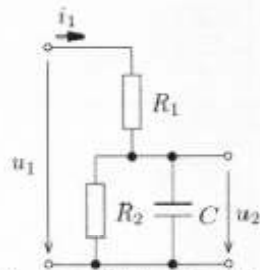
$$H(\omega) = \frac{j\omega}{0.1\text{K} + j\omega 1.1}$$



$R_1 = 100 \Omega, R_2 = 500 \Omega, C = 1 \mu\text{F}, U_0 = 5 \text{V},$
 ~~$U_{ms} = 10 \text{V}, U_{ms} = 20 \text{V}, \omega = 1000 \text{s}^{-1},$~~
 ~~$\varphi_1 = 1/4\pi, \varphi_2 = 1/3\pi$~~

$$Z_c = \frac{R_2 \frac{1}{j\omega C}}{R_2 + \frac{1}{j\omega C}} = \frac{R_2}{1 + j\omega C R_2}$$


$$H(\omega) = \frac{U_2(\omega)}{U_1(\omega)} = \frac{Z_c}{R_1 + Z_c} = \frac{\frac{R_2}{1 + j\omega C R_2}}{R_1 + \frac{R_2}{1 + j\omega C R_2}}$$

$$H(\omega) = \frac{R_2}{R_1(1 + j\omega C R_2) + R_2} = \frac{R_2}{R_1 + R_2 + j\omega C R_1 R_2}$$

$$H(\omega) = \frac{0.5 \text{K}}{0.6 \text{K} + j\omega 10^{-6} \cdot 0.1 \text{K} \cdot 0.5 \text{K}}$$

$$H(\omega) = \frac{0.5 \text{K}}{0.6 \text{K} + j0.05\omega}$$

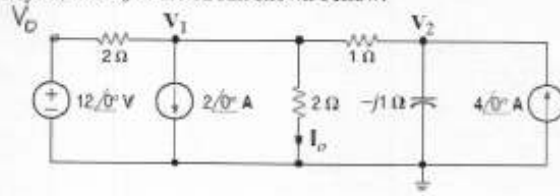Using nodal analysis, find I_0 in the circuit shown below.



$$V_0 = 12 \angle 0^\circ$$

$$\text{Node 1: } \frac{V_1 - V_0}{2} + 2 \angle 0^\circ + \frac{V_1}{2} + \frac{V_1 - V_2}{1} = 0$$

$$\text{Node 2: } \frac{V_2 - V_1}{1} + \frac{V_2}{-j1} - 4 \angle 0^\circ = 0$$

From Node 2 equation we have:

$$V_2 - V_1 + jV_2 - 4 = 0 \Rightarrow V_2(1+j) - V_1 = 4$$

$$V_1 = V_2(1+j) - 4$$

From Node 1 equation:

$$V_1 - V_0 + 4 + \frac{V_1}{2} + 2V_1 - 2V_2 = 0$$

$$V_1 - 12 + 4 + \frac{V_1}{2} + 2V_1 - 2V_2 = 0$$

$$4V_1 - 2V_2 = 8 \Rightarrow 2V_1 - V_2 = 4 \Rightarrow$$

$$2(V_2(1+j) - 4) - V_2 = 0$$


$$2V_2(1+j) - 8 - V_2 = 0$$

$$V_2(1+2j) = 8 \quad V_2 = \frac{8}{1+2j}$$

$$V_1 = \frac{8}{1+2j}(1+j) - 4$$

$$I_0 = \frac{V_1}{2}$$


Find $Z(j\omega)$ for $f=60$ Hz.

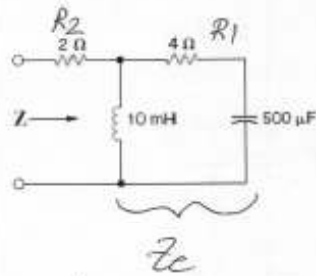

$$Z_e = \frac{j\omega L \left(R_1 + \frac{1}{j\omega C} \right)}{j\omega L + R_1 + \frac{1}{j\omega C}} = \frac{j\omega L (1 + j\omega C R_1)}{1 + j\omega C R_1 - \omega^2 L C}$$

$$Z = R_2 + Z_e = R_2 + \frac{j\omega L (1 + j\omega C R_1)}{1 - \omega^2 L C + j\omega C R_1}$$

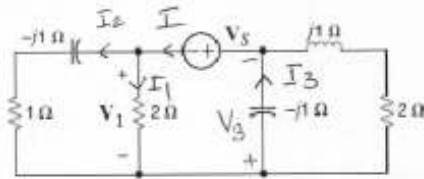Find V_S in the network, if $V_1 = 4 \text{ V}$.



$$V_1 = 4 \text{ V}$$

$$I_1 = \frac{V_1}{2} = \frac{4}{2} = 2$$

$$I_2 = \frac{V_1}{1-j1} = \frac{4}{1-j1} = \frac{4(1+j1)}{(1-j1)(1+j1)} = \frac{4(1+j1)}{2} = 2(1+j1)$$

$$I = I_1 + I_2 = 2 + 2(1+j1) = 4 + j2$$

$$I_3 = I \frac{2+j1}{2+j1-j1} = \frac{2+j1}{2} I$$

$$I_3 = \frac{2+j1}{2} \times (2+j1) = (2+j1)^2$$

$$V_3 = -j1 I_3 = -j(2+j1)^2 =$$

$$= -j(4 + 4j - 1) = -j(3 + 4j) = 4 - 3j$$

$$\text{KVL: } -V_1 - V_S - V_3 = 0$$

$$V_S = -V_1 - V_3 = -4 - (4 - 3j) = -8 + j3$$